

A decorative graphic on the left side of the slide, consisting of white lines and circles on a blue gradient background, resembling a circuit board or a stylized tree structure.

DIGITAL DESIGN

LAB6 COMBINATORIAL CIRCUIT

2021 SUMMER TERM

LAB6

- Verilog
 - Non-blocking assignment , RHS , LHS
 - Intra-statement delay vs Inter-statement delay
 - Sequential block vs Parallel block
- Combinatorial circuit
 - 1bit full adder , 2bits full adder
 - Lighting 7 segment digital tube
- Practice

PRACTICE 1 IN LAB5

```
module testswap( );
    reg temp=0, in2, in1, clock;
    initial begin
        clock = 1'b0;
        forever #50 clock = ~clock;
    end
    initial $display("temp <= in1:    in1 <= in2:    in2 <= temp:");
    always@(posedge clock)
    begin
        $display("=====");
        $display($time, "(display)Before swap: \tin1 = %d, in2 = %d, temp = %d", in1, in2, temp);
        $strobe($time, "(strobe )After swap: \tin1 = %d, in2 = %d, temp = %d", in1, in2, temp);
        temp <= in1;    in1 <= in2;    in2 <= temp;
        $display($time, "(display)After swap: \tin1 = %d, in2 = %d, temp = %d", in1, in2, temp);
    end

    initial begin
        {in1, in2 } = 2'b00;
        repeat(3)
            #100 {in1, in2} = {in1, in2} + 1;
            #100 $finish(0);
        end
endmodule
```

```
temp <= in1;    in1 <= in2;    in2 <= temp;


=====
50(display)Before swap:    in1 = 0, in2 = 0, temp = 0
50(display)After swap:    in1 = 0, in2 = 0, temp = 0
50(strobe )After swap:    in1 = 0, in2 = 0, temp = 0
=====
150(display)Before swap:    in1 = 0, in2 = 1, temp = 0
150(display)After swap:    in1 = 0, in2 = 1, temp = 0
150(strobe )After swap:    in1 = 1, in2 = 0, temp = 0
=====
250(display)Before swap:    in1 = 1, in2 = 1, temp = 0
250(display)After swap:    in1 = 1, in2 = 1, temp = 0
250(strobe )After swap:    in1 = 1, in2 = 0, temp = 1
=====
350(display)Before swap:    in1 = 1, in2 = 1, temp = 1
350(display)After swap:    in1 = 1, in2 = 1, temp = 1
350(strobe )After swap:    in1 = 1, in2 = 1, temp = 1

$finish called at time : 400 ns
```

RHS calculate execute at the very beginning, \$strobe \$monitor execute at end, LHS just before the \$strobe and \$monitor

INTRA-STATEMENT DELAY VS INTER-STATEMENT DELAY

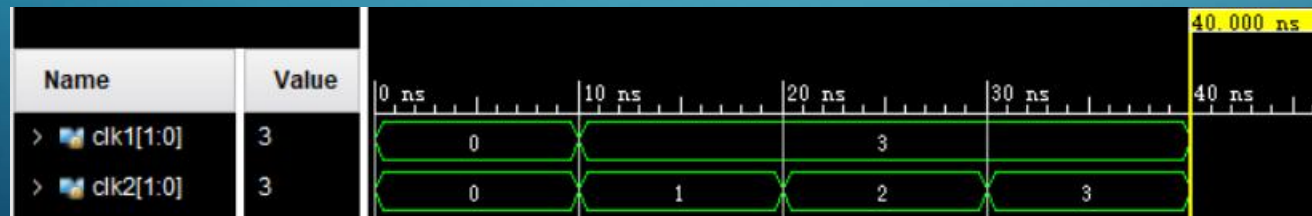- **Intrastatement delay:** happened in a statement
 - such as : `A = #10 1'b0;` //get RHS, delay 10 ,then assign to A
- **Interstatement delay:** happened before the execution of the statement
 - such as: `#10 A=1'b0;` //delay 10, get RHS ,then assignment to A



```
module test_delay();  
    reg [1:0] clk1, clk2;  
    initial  
        {clk1, clk2} = 4'h0;  
  
    initial  
    begin  
        #10 clk2 <= 2'd1;  
        #10 clk2 <= 2'd2;  
        #10 clk2 <= 2'd3;  
    end  
  
    initial  
    begin  
        clk1 <= #10 2'd1;  
        clk1 <= #10 2'd2;  
        clk1 <= #10 2'd3;  
    end  
  
    initial  
        #40 $finish(1);  
endmodule
```

SEQUENTIAL BLOCK VS PARALLEL BLOCK


```
module block();
    reg [1:0] x, y, z;
    initial
    begin
        #10 x = 2' d0;
        #10 x = 2' d1;
        #10 x = 2' d2;
        #10 x = 2' d3;
    end

    initial
    fork
        #10 y = 2' d0;
        #10 y = 2' d1;
        #10 y = 2' d2;
        #10 y = 2' d3;
    join

    initial
    fork
        #10 z = 2' d0;
        #20 z = 2' d1;
        #30 z = 2' d2;
        #40 z = 2' d3;
    join

    initial
    #50 $finish(1);
endmodule
```

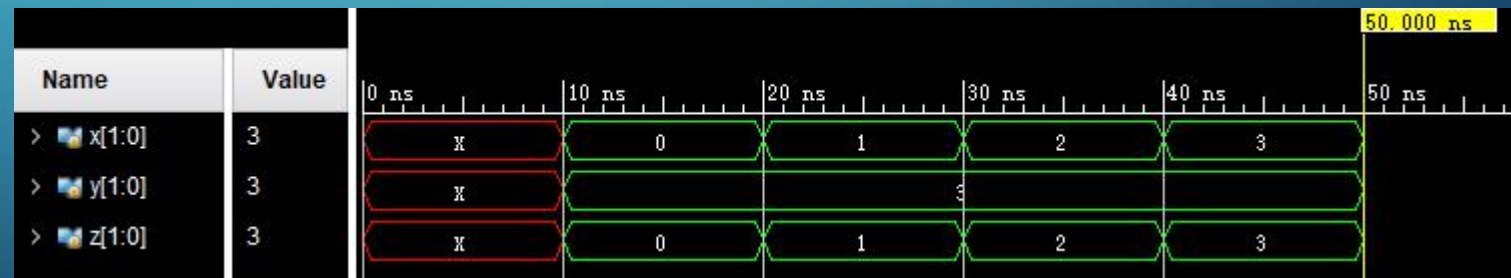- In one module all the block executes at the same time(time 0)
- Sequential block(begin ... end): -----synthesizable
 - all the statements (except unblock assignment) in one sequential block executes with the order of writing.
- Parallel block(fork ... join): -----Not synthesizable
 - all the statement in one parallel block executes at same time



1 BIT FULL ADDER VS MULTI-BITS FULL ADDER


```
module full_add_1b(a, b, cin, sum, cout);
input a, b, cin;
output sum, cout;
assign {cout, sum}=a+b+cin;
endmodule
```

```
module full_add_2b(a, b, cin, sum, cout);
input [1:0]a, b;
input cin;
output[1:0] sum;
output cout;


wire cout1;
full_add_1b u0(a[0], b[0], cin, sum[0], cout1);
full_add_1b u1(a[1], b[1], cout1, sum[1], cout);
endmodule
```

```
module full_add_sm( );
reg scin;
reg [1:0]sa, sb;
wire [1:0]ssum;
wire scout;
full_add_2b u2(sa, sb, scin, ssum, scout);
initial
{scin, sa, sb} = 5'd0;

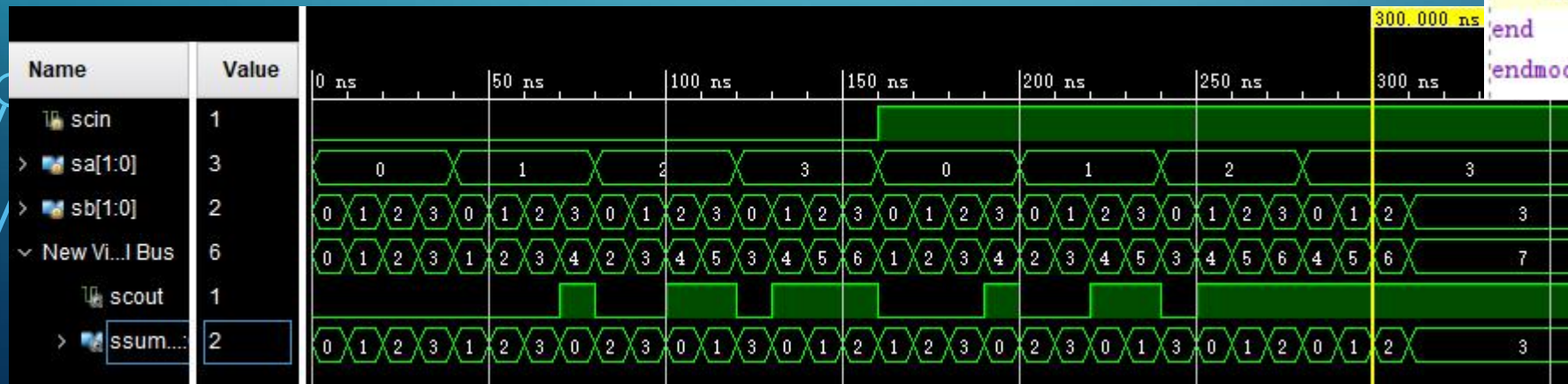
initial
begin
repeat(31)
#10 {scin, sa, sb} = {scin, sa, sb} +1;
end
endmodule
```



LIGHTING A 7-SEG-TUBE

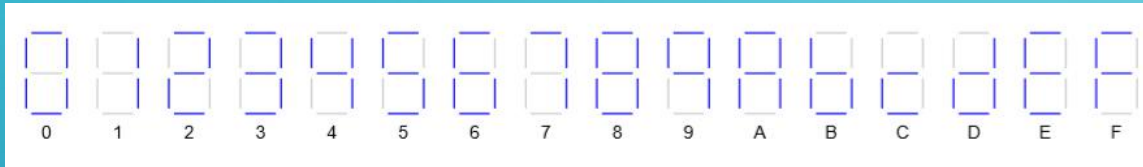

common cathodes

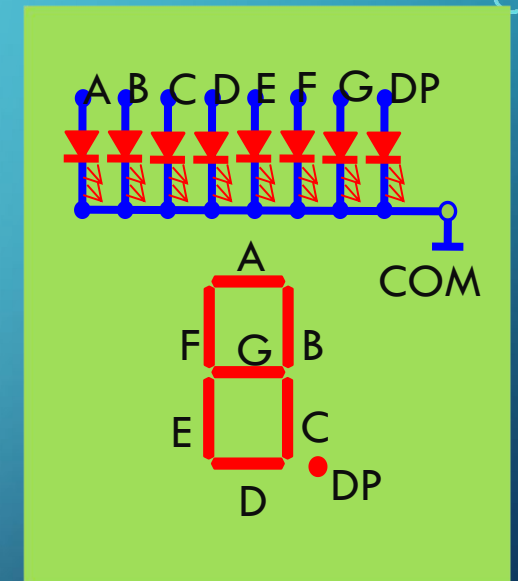

N0				N1			
DK1	DK2	DK3	DK4	DK5	DK6	DK7	DK8
CA0	CB0	CC0	CD0	CE0	CF0	CG0	DP0
CA1	CB1	CC1	CD1	CE1	CF1	CG1	DP1

LIGHTING A 7-SEG-TUBE


- There is an 4-bits width binary number , show its hexadecimal number.
- Using EGO1 develop board
- 4*dial switch are the inputs while 8*7 seg-tubes are the outputs

LIGHTING A 7-SEG-TUBE (DESIGN)

```
assign seg_en = 8'hff;
always @ *
begin
    case(sw)      //A B C D E F G DP
        4'h0: seg_out = 8'b1111_1100; //0
        4'h1: seg_out = 8'b0110_0000; //1
        4'h2: seg_out = 8'b1101_1010; //2
        4'h3: seg_out = 8'b1111_0010; //3
        4'h4: seg_out = 8'b0110_0110; //4
        4'h5: seg_out = 8'b1011_0110; //5
        4'h6: seg_out = 8'b1011_1110; //6
        4'h7: seg_out = 8'b1110_0000; //7

        4'h8: seg_out = 8'b1111_1110; //8
        4'h9: seg_out = 8'b1110_0110; //9
        4'ha: seg_out = 8'b1110_1110; //a
        4'hb: seg_out = 8'b0011_1110; //b
        4'hc: seg_out = 8'b0001_1010; //c
        4'hd: seg_out = 8'b0111_1010; //d
        4'he: seg_out = 8'b1001_1110; //e
        4'hf: seg_out = 8'b1000_1110; //f

        default: seg_out = 8'b0000_0000; //all disabled
    endcase
end
```

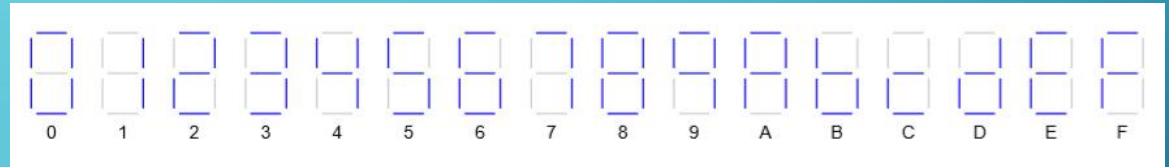

Eight 7-seg-tubes, each one has a enable pin, while it's 1 it enable the corresponding tube, while it's 0 it disable the tube

While 'seg_en' is 8'hff, it means enable all the tubes

From DP to CA ~CG, all are positive enable

LIGHTING A 7-SEG-TUBE (CONSTRAINTS FILE)

- I/O Planning: choose LVCMOS33*
- Use SW7, SW6, SW5, SW4 as sw[3:0] input pins
- Select pins on eight 7-seg tubes
 - Use DK1, DK2, DK3, DK4 as seg_en[7:0] output pins
- Use CA0, CB0, CC0, CD0, CE0, CF0, CG0, DP0 as seg_out[7:0] output pins




LVCMOS33*

sw (4)	
<input checked="" type="checkbox"/> sw[3]	P5
<input checked="" type="checkbox"/> sw[2]	P4
<input checked="" type="checkbox"/> sw[1]	P3
<input checked="" type="checkbox"/> sw[0]	P2

seg_en (8)	
<input checked="" type="checkbox"/> seg_en[7]	G2
<input checked="" type="checkbox"/> seg_en[6]	C2
<input checked="" type="checkbox"/> seg_en[5]	C1
<input checked="" type="checkbox"/> seg_en[4]	H1
<input checked="" type="checkbox"/> seg_en[3]	G1
<input checked="" type="checkbox"/> seg_en[2]	F1
<input checked="" type="checkbox"/> seg_en[1]	E1
<input checked="" type="checkbox"/> seg_en[0]	G6


seg_out (8)	
<input checked="" type="checkbox"/> seg_out[7]	B4
<input checked="" type="checkbox"/> seg_out[6]	A4
<input checked="" type="checkbox"/> seg_out[5]	A3
<input checked="" type="checkbox"/> seg_out[4]	B1
<input checked="" type="checkbox"/> seg_out[3]	A1
<input checked="" type="checkbox"/> seg_out[2]	B3
<input checked="" type="checkbox"/> seg_out[1]	B2
<input checked="" type="checkbox"/> seg_out[0]	D5

LIGHTING A 7-SEG-TUBE (TESTING RESULT)

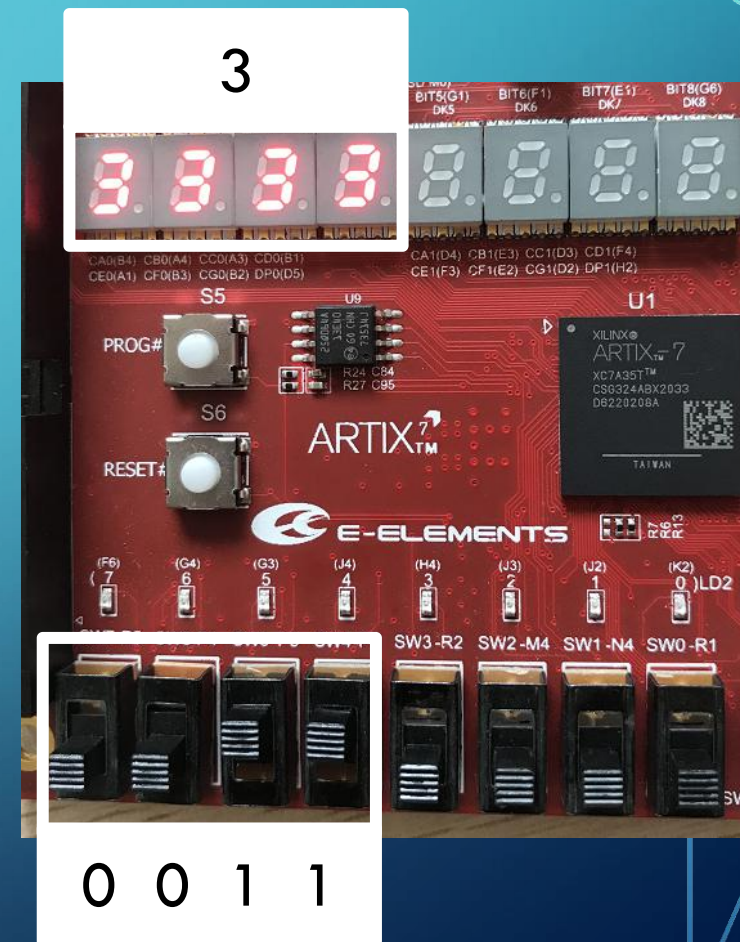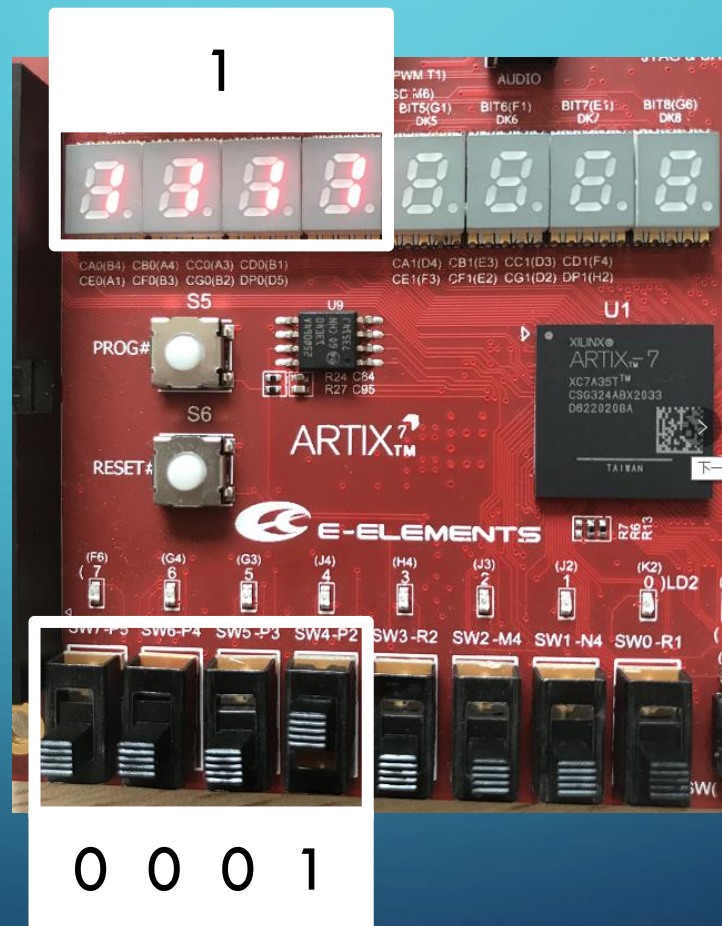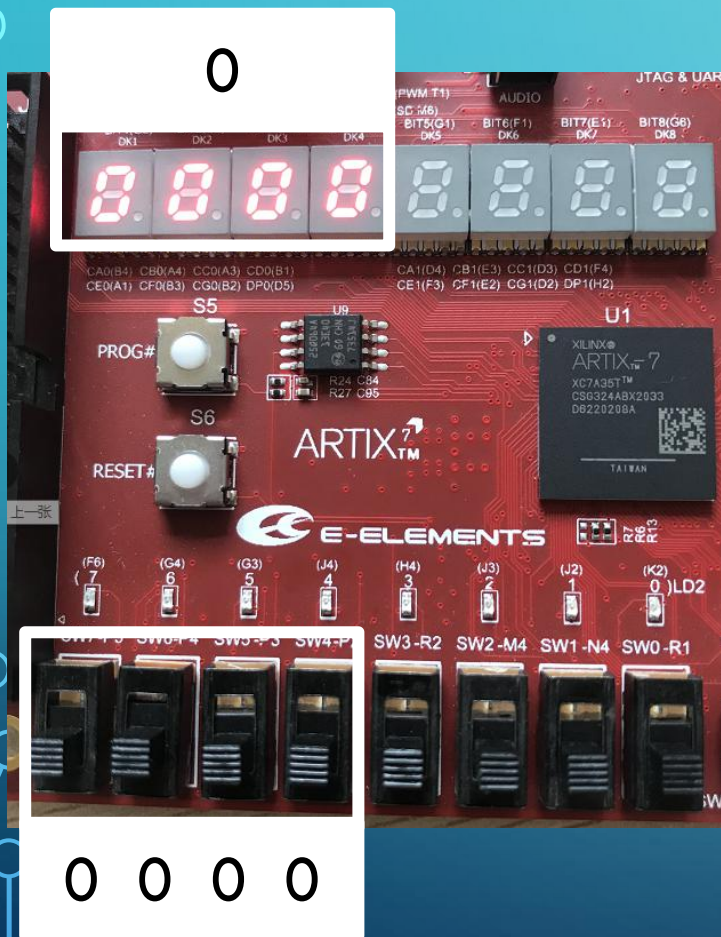

PRACTICE 1

- In the 7-seg tub demo, the other 4 tubes are not driven, please complement the demo to control them with the switches.
- Do the design and verify the function of your design.
- Create the constrain file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the EGO1 develop board.

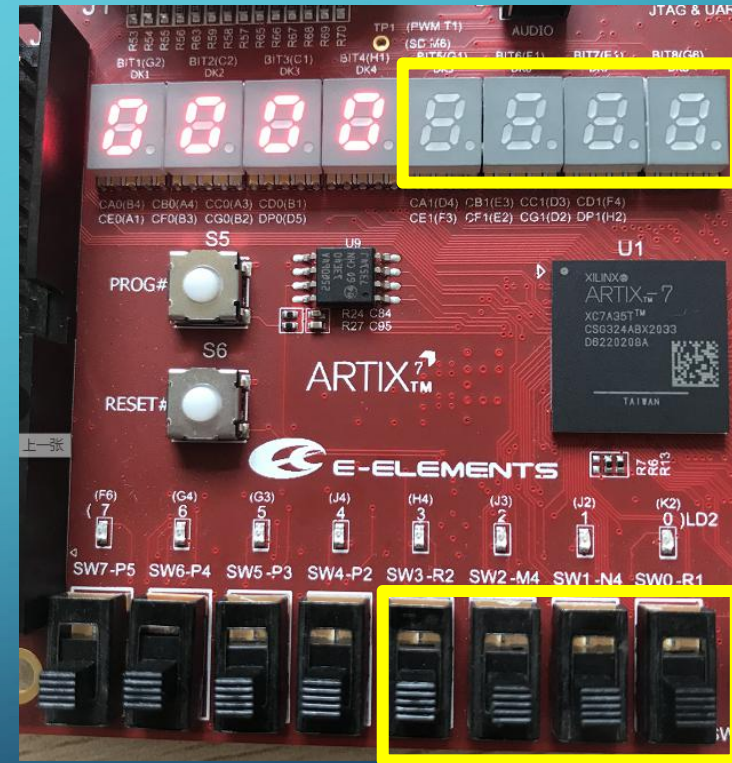

PRACTICE 2

- There are sixteen wards, which are numbered from 0 to F respectively, among which #0 ward has the lowest priority, #F has the highest priority(Priority increases as the number increases). Each room has an call bell, it could be turn on or turn off. In the main control room there is a display screen which shows the ID of the room whose bell is on with highest priority of all the bell on room.
- Please write a circuit to implement this function and test.
 - Do the design and verify the function of your design.
 - Create the constrain file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the EGO1 develop board.